

ART2040

Electronics & Physical Computing



Concepts

- ❑ Transducers (sensors/actuators)
Convert between physical/electrical energy
- ❑ Input/Output
Direction of energy flow
- ❑ Analog/Digital
Continuous (i.e. multi-state) vs Binary (i.e. two-state)
- ❑ Serial/Parallel
How events in the flow occur over time

Interaction (break into 3 steps)

- Input (listen)
- Processing (think)
- Output (speak)

Example: movement -> light & sound

Transduction (Transducers)

- Eyes, ears, hands, mouth of physical computing systems
- Input transducers: sensors
- Output transducers: actuators

- Challenge: convert physical energy (light, heat, sound, pressure) to electrical energy and vice versa

Analog & Digital


- Analog has continuous range or multiple states
i.e. gas pedal of a car
- Digital has only two states: on/off
i.e. a light switch

Parallel & Serial

How are we listening/speaking?

- Serial: events occur one at a time
- Parallel: two or more events occur at the same time

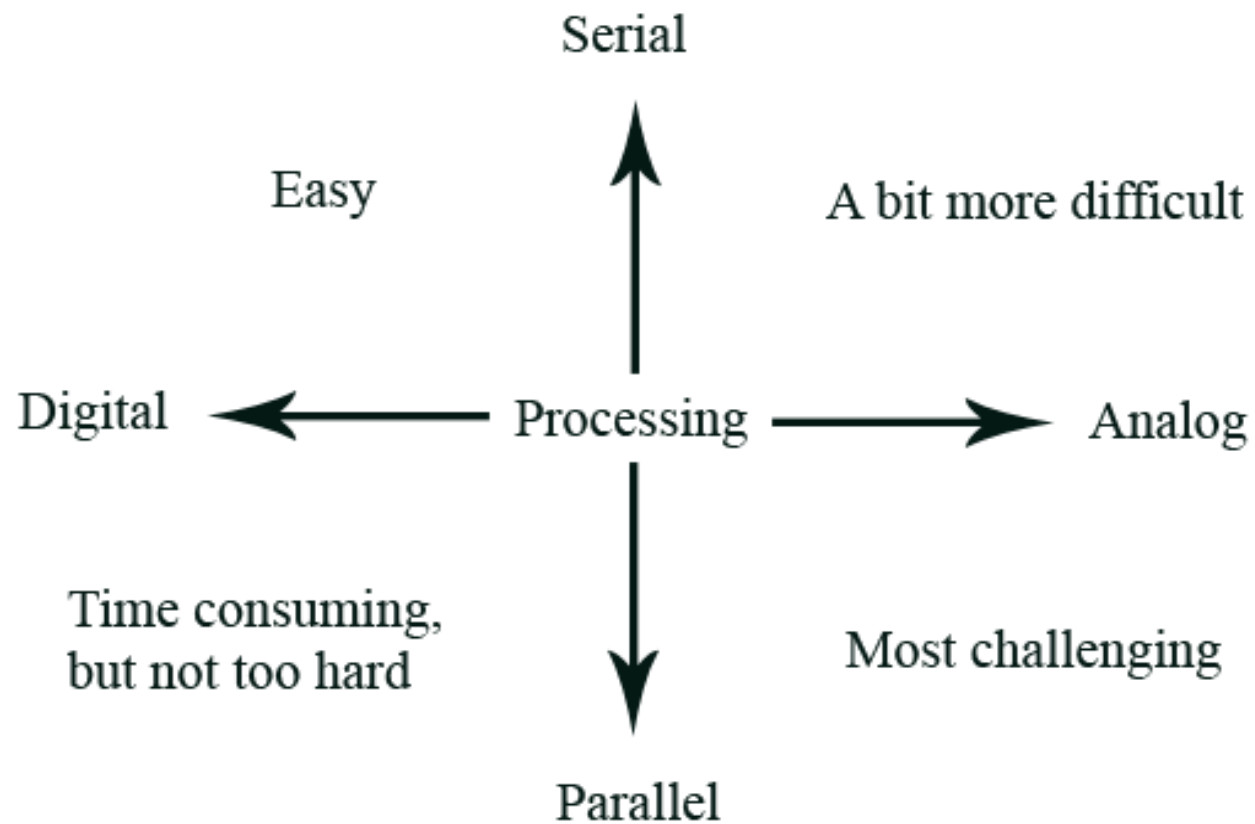Note: this also applies to electrical flow in circuits



Getting Started

- First describe *what* happens, not *how* it happens (avoid describing specific technologies – this comes later)
- Break down into input, output, and processing
- Identify inputs & outputs as analog or digital

Refer to example: movement -> light & sound

Levels of Abstraction

Food	Software	Circuits
<ul style="list-style-type: none">□ Highest level: go to restaurant□ TV Dinners□ Hamburger Helper□ Supermarket□ Growing own food□ Lowest level: "Henry, go kill me a chicken and we'll have some pot pie tonight"	<ul style="list-style-type: none">□ MAX,MSP□ Puredata □ Java□ C □ ASSEMBLY□ MACHINE Language ("100100101110")	<ul style="list-style-type: none">□ Buy readymade circuit □ Build circuit on breadboard□ Build/etch your own PCB□ Physically build your own components and circuit

The Tools

- **Circuits:** glue between sensors\actuators & computers
- **Computers:**
 1. Microcontrollers (Arduino) - receive info from sensors, control other devices (i.e. motors), communicate with PCs
 2. Desktop Computers (i.e. PCs) – run programs like PD
- **Programming:**
 1. Puredata
 2. Arduino Programming Environment

Electricity

- Flow of electrons from a point of greater electrical energy to a point of lesser electrical energy
- Always follows path of least resistance
- A circuit is a closed loop containing an electrical source (i.e. battery) and a load (i.e. light bulb)

Current/Voltage/Resistance

- Voltage (Volt) – is the difference of electrical energy between two points
- Current (Amps) – is the amount of electrical energy passing through any given point
- Resistance (Ohms) – is the amount that a component resists current flow

Ohm's Law

- Relationship between voltage, current, resistance

Voltage = Current x Resistance

Likewise: Current = Voltage/Resistance

Resistance = Voltage/Current

Electrical Power (Wattage)

- ❑ Determines how much “work” a circuit can do (i.e. turning a motor to lift a weight takes more power than turning on a small light)
- ❑ Power is measured in Watts
- ❑ $\text{Power (Watts)} = \text{Voltage (Volts)} \times \text{Current (Amps)}$



Two ways to supply electrical power:

1. Direct Current (DC) has constant voltage/current. Batteries supply DC.
 2. Alternating Current (AC) alternates voltage in a wave pattern (usually sine).
- Most electronics operating using DC. Electricity supplied to homes is AC therefore we need AC-to-DC converters (transformers) or use batteries.

Circuits


- Current flows from positive terminal to negative terminal (ground). Along the way you insert various components (i.e. resistors, capacitors, diodes) to divert the electrons to do your bidding

Circuits

- ❑ Remember: electricity always favors path of least resistance (avoid short circuits!)
- ❑ Also: all the electrical energy (voltage) supplied must be used up in the circuit. If too much energy is supplied components heat up and break!

Resistors




- Give electricity something to do: convert electrical energy to heat (preventing short circuits)
- No polarity (no positive/negative side)
- Measured in ohms, indicated how much resistance they offer
- Schematic symbol: 

Variable Resistors

- Commonly used as sensors for analog input.

- Photocells:  resistance changes with change in light levels

- Thermistor:  resistance changes with change in heat



Potentiometer aka Pot (another variable Resistor)




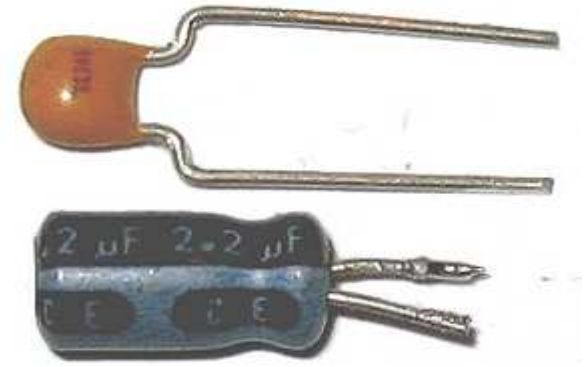
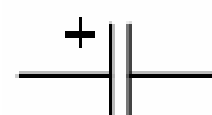
- ❑ Changes resistance by turning knob (commonly used as volume knobs)
- ❑ Orientation is important: they have three pins

- ❑ Schematic symbol:



Capacitors




- ❑ Store electrical energy (charge)
- ❑ Measured in farads (F). Most capacitors are in the range of microfarads (mF or μF), picofarads (pF), nanofarads (nF).
- ❑ Some are unpolarized: 
- ❑ Some are polarized: 
+ goes towards higher voltage


-
- Capacitors are good for smoothing out erratic electrical flow: they release charge when current dips and store excess charge when the current spikes.


Inductors

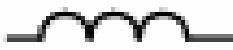


- ❑ Coil of wire wrapped around a core (air, iron, other magnetic metals)
- ❑ Property of inductance: electrical current produces a magnetic field
- ❑ Analogous to capacitors: an inductor can be considered as an inverse of a capacitor
- ❑ Measured in Henries (H), 


Diodes

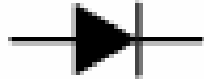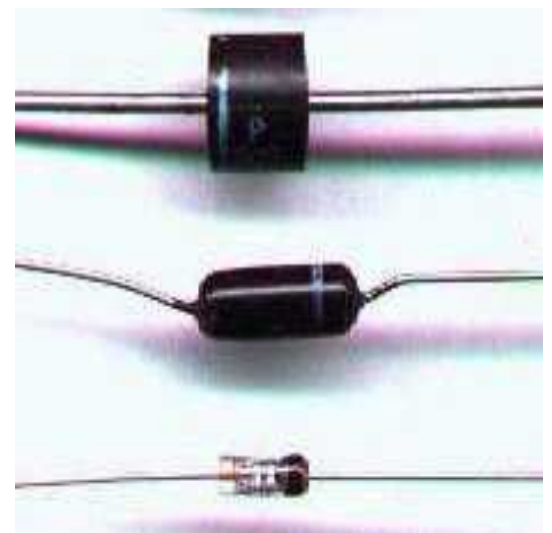- ❑ It's like a one way street: only allows current to flow in one direction
- ❑ This means they are polarized (orientation matters)
- ❑ Schematic Symbol: 



LED (Light Emitting Diode)

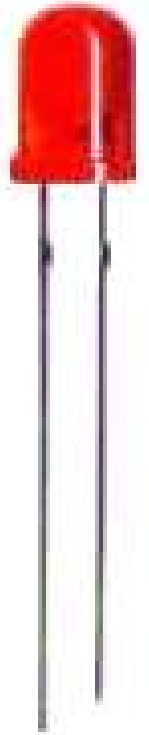- Low power 'light bulb' 
- Usually rated at or below 5V and 20milliamps (0.02A)
- Infrared (IR) LEDs emit infrared light (TV remotes). Good for simple wireless communication




Switches


- Simple concept, but many varieties
- Normally open (N.O.) vs normally closed (N.C)
- Momentary (pushbuttons) vs toggle (light switch)
- Magnetic switches (reed switches)




SPST toggle
normally open



Pushbutton
normally open

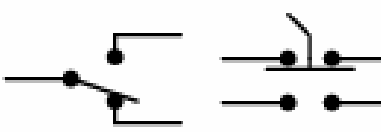

SPDT toggle

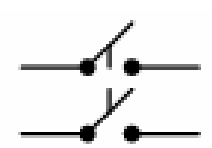


DPST toggle


Transistors and Relays



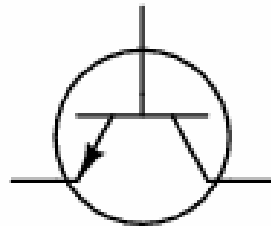- ❑ Switching devices controlled by electronic signals (as opposed to physical)
- ❑ Relays work by passing small current through a coil to activate a switch that allows large current to pass
- ❑ Transistors are a bit more complicated




NPN Transistor

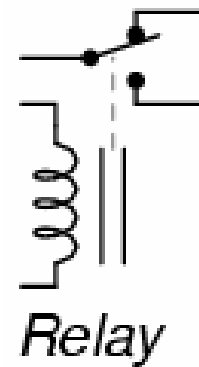

Relay

example

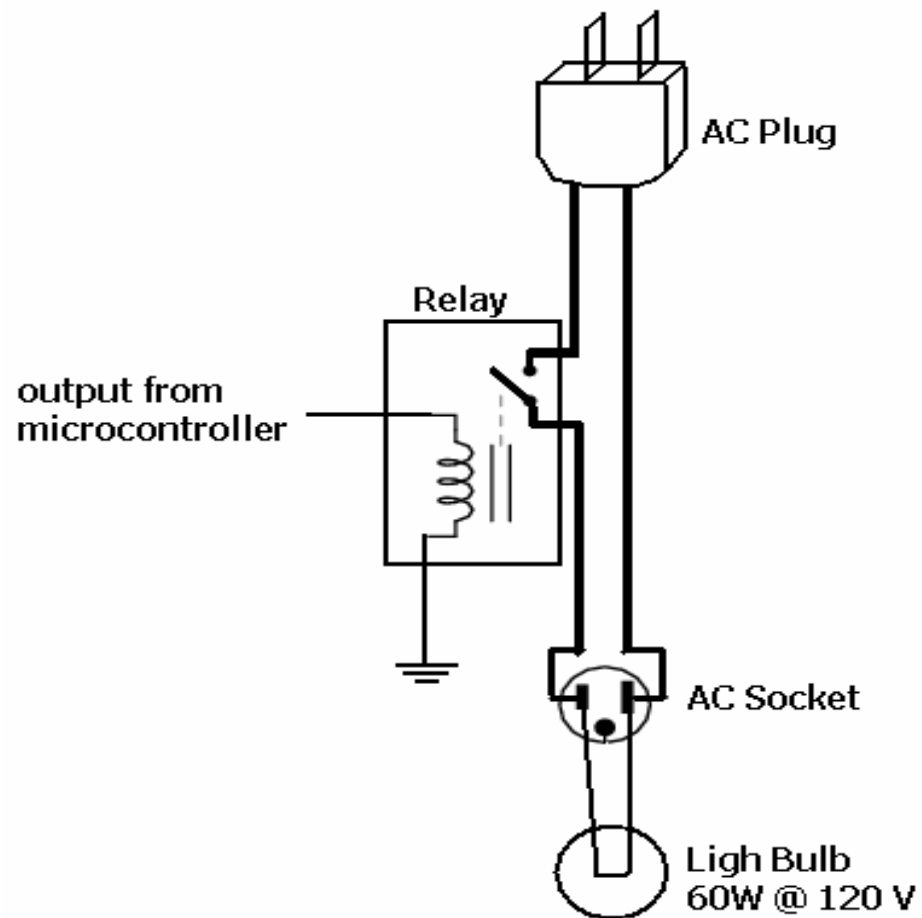

Motors: RC Servo

- ❑ Unlike traditional motors
- ❑ Built in components let user control exact position of the motor
- ❑ Use Pulse Width Modulation (PWM) signal to control the motor (PWM is obtained from microcontroller)
- ❑ Easy to control (compared to other motors)





Solenoids



- ❑ Device that provides linear motion
- ❑ Coil of wire with iron shaft
- ❑ Uses property of inductance to generate magnetic field and shaft is pulled or pushed as a result
- ❑ Not very difficult to control (usually requires relay/transistor and diode)

Voltage Regulators

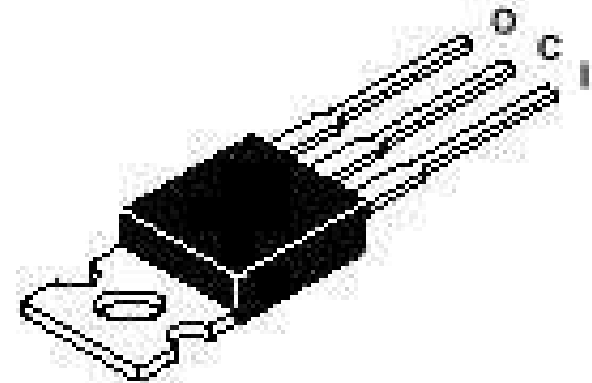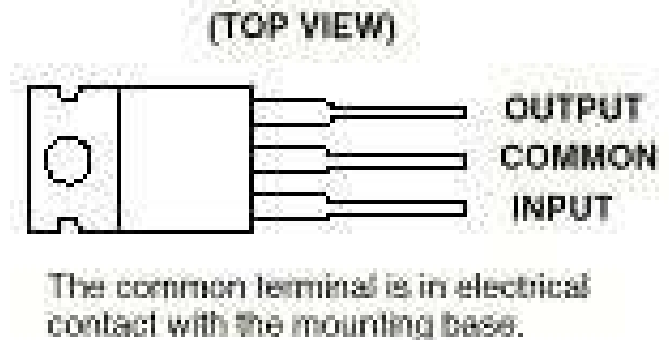- ❑ convert a range of voltages (8-15V DC) to a fixed voltage (5V DC)
- ❑ Common regulator is the 7805 which converts to 5V DC rated for 1Amp




Other components/Tools

- ❑ Connectors: male, female (note: connectors emitting electrical energy should be female)
- ❑ Multimeter:
Measures voltage, current, resistance, sometimes even capacitance





Microcontrollers (Arduino board)

- www.arduino.cc

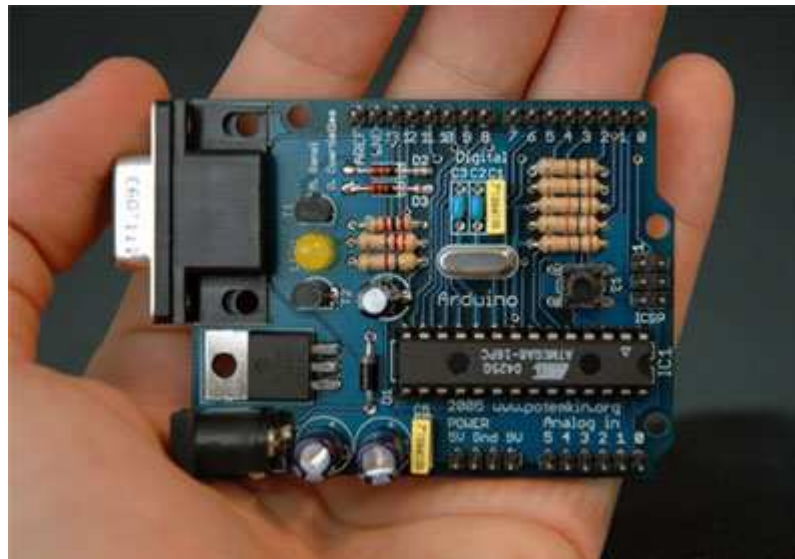

Building a circuit: Working from a Schematic

- Lets make a Theremin

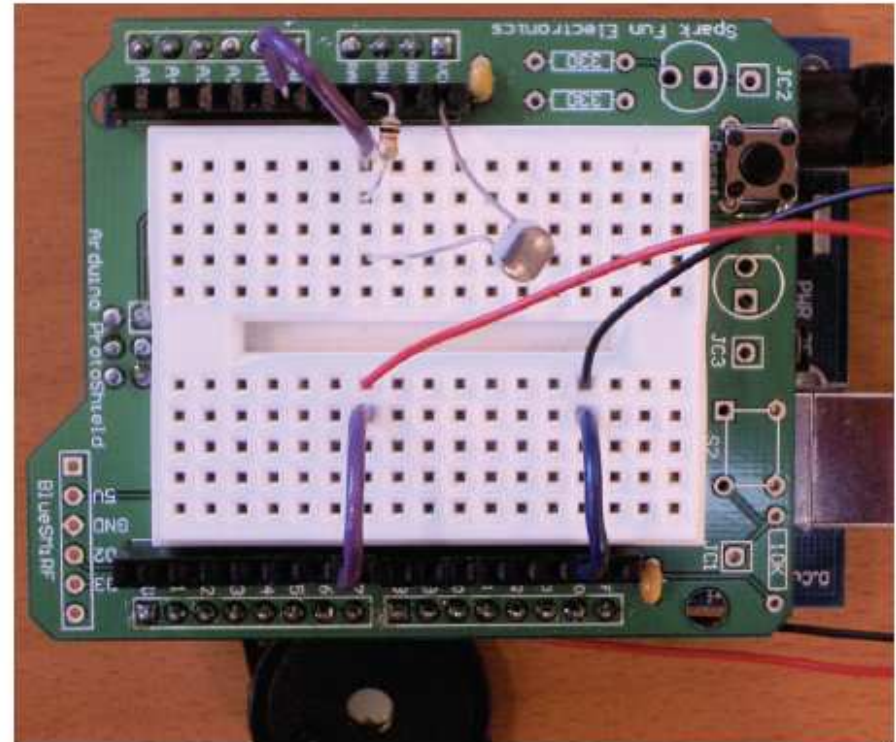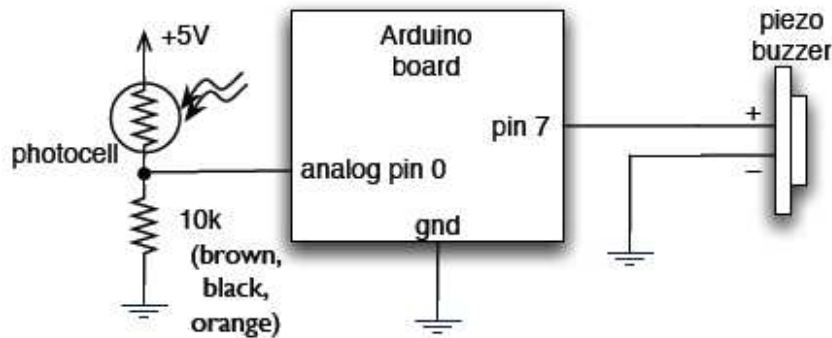

“theremin”

Move hand over
photocell to
change pitch

Play with val processing & cycles count
to alter sensitivity, pitch and timbre

This is *frequency modulation*,
since you're changing the frequency



The screenshot shows the Arduino IDE interface. The title bar reads "Arduino - 0005 Alpha". The menu bar includes icons for running, stopping, saving, opening, uploading, and downloading. The sketch is named "theremin". The code is as follows:

```
pinMode(speakerPin, OUTPUT);
beginSerial(9600);
Serial.println("ready");
}

void loop() {
  digitalWrite(speakerPin, LOW);

  val = analogRead(potPin);    // read value from the sensor
  val = val*2;                 // process the value a little
  //val = val/2;               // process the value a little

  for( int i=0; i<50; i++ ) { // play it for 50 cycles
    digitalWrite(speakerPin, HIGH);
    delayMicroseconds(val);
    digitalWrite(speakerPin, LOW);
    delayMicroseconds(val);
  }
}
```

Below the code editor, a status bar indicates "Done uploading." and a serial monitor window shows the following output:

```
Atmel AVR ATmega8 is found.
Uploading: flash
Firmware Version: 1.18
Firmware Version: 1.18
```

The serial monitor shows a line number "2" at the bottom.

Resources

- *Physical Computing* by Dan O'Sullivan and Tom Igoe
 - <http://electronics.howstuffworks.com>
-